

2020

ELECTRONICS — HONOURS

Paper : CC-6

Full Marks : 50

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **question no. 1** and **any four** from the rest, taking **two** from **Unit-I** and **two** from **Unit-II**.

1. Answer **any ten** questions :

1×10

- (a) h_{ie} is a/an
- | | |
|-------------------------|---------------------------|
| (i) impedance parameter | (ii) admittance parameter |
| (iii) hybrid parameter | (iv) Z-parameter. |
- (b) Output impedance of an amplifier equals the ratio of
- | | |
|---------------------------------------|--|
| (i) output voltage to input voltage | (ii) input voltage to output voltage |
| (iii) output current to input current | (iv) output voltage to output current. |
- (c) MOSFET stands for
- | | |
|--|---|
| (i) Metal On Semiconductor Field Effect Transistor | (ii) Metal Oxide Switch Field Effect Transistor |
| (iii) Metal Oxide Switch Full Effect Transistor | (iv) Metal Oxide Semiconductor Field Effect Transistor. |
- (d) When a transistor is used as a switch, it is operated in the
- | | |
|-----------------------------------|-------------------------------------|
| (i) active and saturation regions | (ii) cut-off and saturation regions |
| (iii) cut-off and active regions | (iv) all of the above regions. |
- (e) A power-amplifier is a
- | | |
|-------------------------------|-----------------------------|
| (i) large signal amplifier | (ii) small signal amplifier |
| (iii) medium signal amplifier | (iv) none of these |
- (f) Negative feedback in an amplifier
- | | |
|--|---|
| (i) decreases gain and decreases bandwidth | (ii) decreases gain and increases bandwidth |
| (iii) increases gain and decreases bandwidth | (iv) none of the above. |

Please Turn Over

(g) A tuned oscillator is

- (i) a R-C oscillator
- (ii) an L-C oscillator
- (iii) an L-R oscillator
- (iv) none of (i), (ii) and (iii).


(h) A Rectifier circuit converts

- (i) a.c to d.c.
- (ii) d.c to a.c.
- (iii) low frequency a.c. to high frequency a.c.
- (iv) none of the above.




(i) The different stages in a regulated power supply are (a) step-down transformer (b) rectifier (c) filter (d) regulator. Arrange them in the order they appear.

- (i) (a), (b), (c), (d)
- (ii) (b), (d), (a), (c)
- (iii) (a), (b), (d), (c)
- (iv) None of these.

(j) The following circuit :

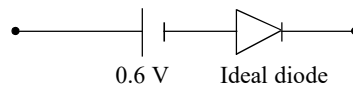

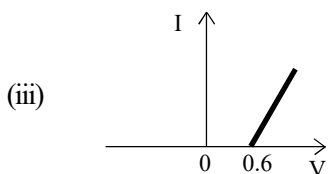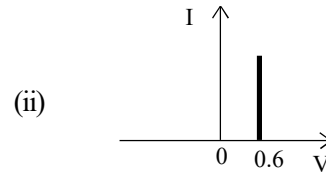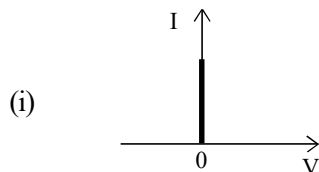is an equivalent representation of which of the following piecewise linear models of a p-n diode :



(iv) None of (i), (ii) and (iii).

(k) The point of intersection of the load-line and the diode-characteristic curve is called the 'Q-point'. The letter Q stands for

- (i) Quiet
- (ii) Quiescent
- (iii) Quality
- (iv) None of (i), (ii) and (iii).

(l) 'Pinch-off' voltage is related to :

- (i) p-n diode
- (ii) JFET
- (iii) BJT
- (iv) zener-diode.

Unit - I

2. What is a Diode Clamper? Why is it used? Explain the working of a bridge rectifier with the help of a circuit diagram. 2+2+4+2
3. (a) What is meant by biasing with reference to a transistor circuit?
(b) Explain in brief the working of collector-to-base bias in a transistor circuit.
(c) Explain with a diagram how stability is achieved in a self-bias transistor circuit. 2+4+4
4. What do you mean by hybrid parameters of a transistor amplifier in CE configuration? Derive the expression for input impedance, forward current gain, forward voltage gain and output impedance in terms of the four hybrid parameters. 2+(2+2+2+2)
5. Draw a neat diagram of a JFET. Explain the working of a JFET. Write down the expression relating g_m with V_{GS} . Explain the relationship. 3+3+2+2

Unit – II

6. What is negative feedback? Explain the advantages of negative feedback. How does negative feedback reduce distortion? Why is positive feedback used? 2+3+3+2
7. (a) How is a power amplifier different from a small-signal amplifier? Name the different types of power amplifiers and explain their working with the help of output waveforms.
(b) What do you mean by efficiency of a power amplifier?
(c) What is cross-over distortion in an amplifier? (2+4)+2+2
8. (a) Give two examples each of R-C and L-C type oscillators.
(b) What is a regulated power supply?
(c) Explain with a circuit diagram the working of a two-transistor series regulator circuit. 2+2+(4+2)
-