

2020

ELECTRONICS — HONOURS

Paper : DSE-B-2

(Power Electronics)

Full Marks : 50

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **question no. 1** and **any four** questions from the rest.

1. Answer **any ten** questions :

1×10

- (a) When anode is positive with respect to cathode in an SCR, the no. of reverse biased junction is/are
- | | |
|---------|---------|
| (i) 1 | (ii) 2 |
| (iii) 3 | (iv) 4. |
- (b) In a thyristor, anode current is caused due to
- | | |
|--------------------------|--------------------------|
| (i) electrons | (ii) electrons and holes |
| (iii) electrons or holes | (iv) holes only. |
- (c) A thyristor, when triggered, changes from forward blocking state to conduction state if its anode to cathode voltage is equal to
- | | |
|-----------------|------------------|
| (i) V_{DRM} | (ii) V_{DSM} |
| (iii) V_{RRM} | (iv) V_{RSM} . |
- (d) In an SCR, holding current is
- | | |
|----------------------------------|---------------------------------------|
| (i) equal to latching current | (ii) greater than latching current |
| (iii) less than latching current | (iv) not related to latching current. |
- (e) During forward blocking state, the thyristor is associated with
- | | |
|------------------------------------|------------------------------------|
| (i) large current, low voltage | (ii) high voltage, low current |
| (iii) medium voltage, high current | (iv) medium current, high voltage. |
- (f) A thyristor may be termed as
- | | |
|--------------------------|--------------------------|
| (i) DC switch | (ii) AC switch |
| (iii) either (i) or (ii) | (iv) square wave switch. |

Please Turn Over

- (g) A forward voltage may be applied to a thyristor after its
- (i) anode current reduces to zero
 - (ii) gate recovery time
 - (iii) reverse recovery time
 - (iv) anode voltage reduces to zero.
- (h) The $\frac{di}{dt}$ rating of an SCR is specified for its
- (i) decaying anode current
 - (ii) decaying gate current
 - (iii) rising gate current
 - (iv) rising anode current.
- (i) The $\frac{dv}{dt}$ limitation of a thyristor can be improved by connecting a RC network across the thyristor, which is called
- (i) Turn-on snubber
 - (ii) Turn-off snubber
 - (iii) Series snubber
 - (iv) Parallel snubber.
- (j) The switching speed and on-state losses of a thyristor is
- (i) directly proportional to the width of n_1 region
 - (ii) inversely proportional to the width of n_1 region
 - (iii) directly proportional to the width of n_2 region
 - (iv) directly proportional to the anode current.
- (k) In the case of power BJT, the period from the end of positive base (switching) current until the device enters linear (active) region is called
- (i) saturation time
 - (ii) rise time
 - (iii) transit time
 - (iv) delay time.
- (l) The power MOSFETs are
- (i) current controlled devices
 - (ii) voltage controlled devices
 - (iii) resistive controlled devices
 - (iv) inductive controlled devices.
2. (a) Define latching current and holding current as applicable to an SCR. Show these currents on its static I–V characteristics.
- (b) What are the necessary conditions for turning-on of an SCR? Discuss. (2+2+2)+4
3. (a) Explain the constructional details of IGBT and its I–V characteristics.
- (b) Draw the two transistor equivalent circuit for an IGBT and explain it briefly. (3+2)+(3+2)
4. (a) “Every rectifier is a converter but every converter need not be a rectifier.”— Explain the statement.
- (b) Define ‘Firing angle’.
- (c) With a neat circuit diagram, explain the working of a single phase controlled rectifier with resistive load. Show the input and output waveforms. 2+1+(2+4+1)

5. (a) Draw a neat diagram and explain the constructional details of a power MOSFET.
(b) Explain the switching characteristics of a power MOSFET with a neat diagram. (2+4)+(3+1)
6. (a) Define an inverter.
(b) Write down the classification of inverters.
(c) With a neat circuit diagram briefly explain the working of a series inverter. 2+2+(1+5)
7. (a) How do you classify DC choppers on the basis of the following?
(i) According to the input / output voltage levels.
(ii) According to the directions of output voltage and current.
(iii) According to circuit operation.
(iv) According to commutation methods.
(b) With a neat circuit diagram explain the operation principle of step-up / down choppers. 4+(2+4)
8. (a) With a neat circuit diagram briefly explain the working of a Boost type converter.
(b) Why is a CuK converter better than Buck-Boost converter? (2+5)+3
-