

**2020**

**ELECTRONICS — HONOURS**

**Paper : SEC-A-2**

**(Circuit Modeling using PSPICE)**

**Full Marks : 80**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**Group - A**

1. Answer **any ten** questions from the following : 2×10
- (a) State any two drawbacks of PSpice software.
  - (b) Explain ·STEP control statement.
  - (c) Describe the ·TEMP control statement in brief.
  - (d) How do you represent a CCVS device in PSpice?
  - (e) What do you mean by DC sweep in PSpice?
  - (f) Explain ·TF control statement in brief.
  - (g) How do you represent a BJT in PSpice?
  - (h) How do you represent a P-N diode in PSpice?
  - (i) Explain ·OP control statement.
  - (j) How do you represent independent DC voltage and independent DC current sources in PSpice?
  - (k) Write the general form of exponential sources in PSpice.
  - (l) How do you represent a resistor and a capacitor in PSpice?

**Group - B**

Answer **any four** questions.

5×4

- 2. Write a PSpice netlist to obtain the output voltage of a series negative clipper using *p-n* diode.
- 3. How do you represent a JFET and a MOSFET in PSpice?
- 4. Write down a PSpice netlist to obtain the voltage across load resistance of a half wave rectifier using a capacitor filter.
- 5. Write a PSpice netlist to obtain the current through a reverse biased Zener diode and to plot the I-V characteristics.


**Please Turn Over**

6. Write a PSpice netlist to obtain the output characteristics of a BJT in CE mode.
7. Describe the different file formats used in PSpice.


**Group - C**

Answer *any four* questions.

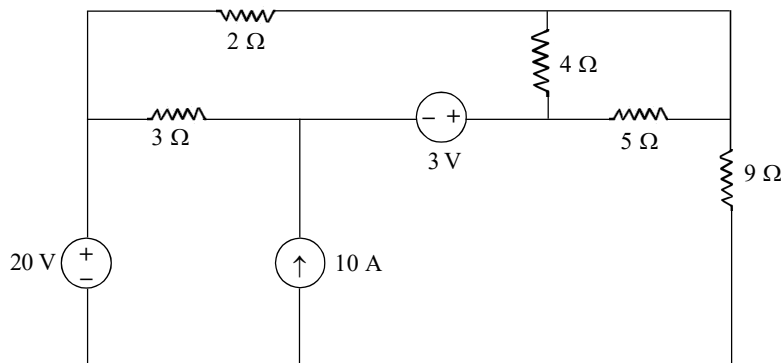
8. Explain the function of ·PROBE and ·PLOT statements. Write the PSpice netlist for the following circuit for DC analysis. 4+6



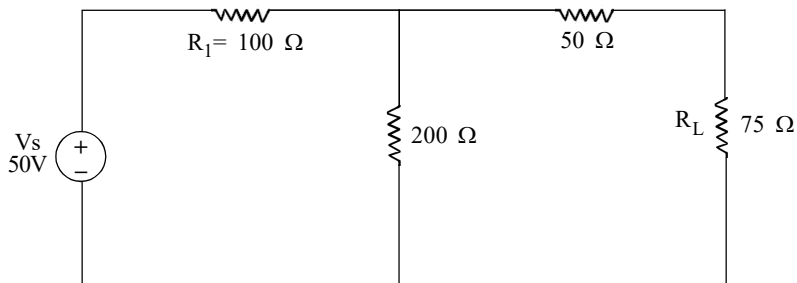
9. Write the PSpice netlist for the following circuit to obtain voltage across  $R_L$  and current through  $R_1$ . Vary  $V_S$  from 0 to 50V in 2V steps. Use ·PRINT command. 7+3



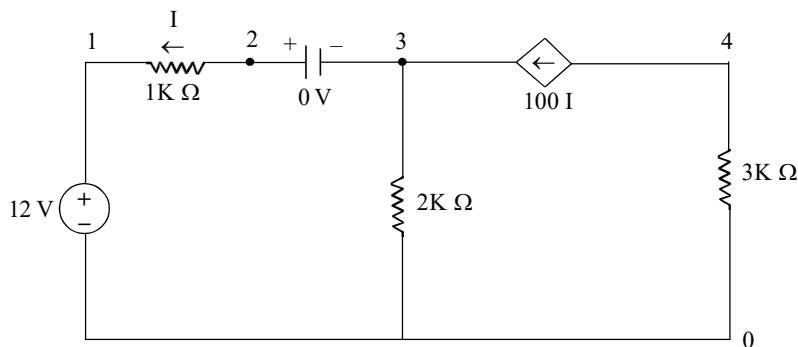
10. What is a VCVS? How do you represent it in PSpice? Write a PSpice netlist for the circuit given bellow to determine the voltages at nodes 2 and 3 and the current  $- (I)$  through the  $1k\Omega$  resistance. 1+2+7



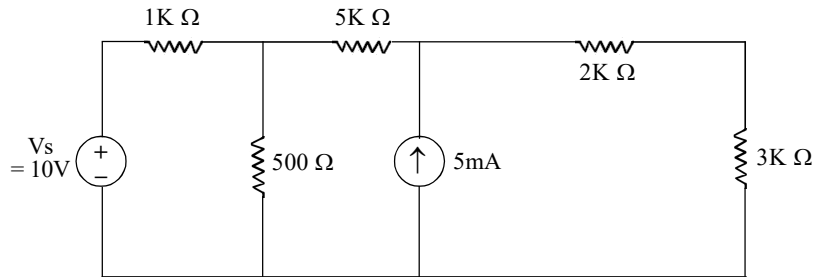11. Write the PSpice netlist for the following circuit using `·DC`, `·PRINT`, `·PROBE` and `·PLOT` statements. Vary  $V_s$  from 0 to 10V in 1V steps. 7+3



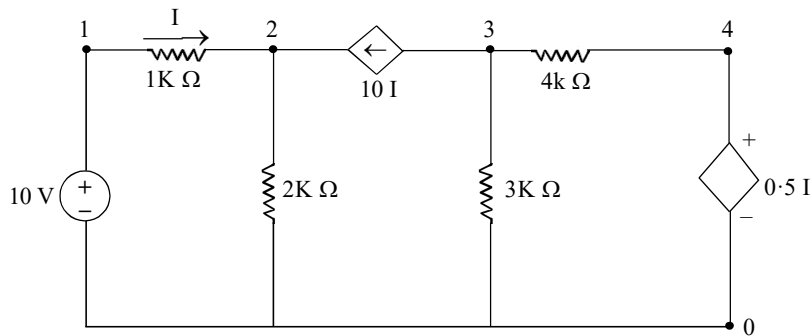12. Describe `·TRAN` statement in PSpice. Write the PSpice netlist to perform the DC analysis for the following circuit. Also find current ( $I$ ) through the  $1k\Omega$  resistor and the voltage at node 4. 3+7



13. How do you represent a sinusoidal AC source in PSpice? Write a PSpice netlist for the following RC circuit and find the magnitude of the current, its real and imaginary components and its phase with respect to the source. 3+7

