

2021

COMPUTER SCIENCE — HONOURS

Paper : CC-4

(Basic Electronic Devices and Circuits)

Full Marks : 50

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **question No. 1** and **any four** from the rest.

1. Answer **any five** questions: 2×5
- (a) What is the difference between Avalanche breakdown and Zener breakdown of a $p - n$ junction?
 - (b) State the function of the depletion region of a $p - n$ junction diode.
 - (c) Explain the term 'peak inverse voltage'.
 - (d) State how FET can be used as VVR.
 - (e) State the relation between α and β of a transistor.
 - (f) Differentiate static and dynamic MOS cell.
 - (g) What CMRR of an OPAMP?
 - (h) What is the difference between 'Enhancement' type and 'Depletion' type MOSFET?
2. (a) State and explain Norton's theorem.
- (b) Define the cut-in voltage of a $p - n$ junction diode. What are its typical values for Ge and Si diodes?
- (c) Draw the circuit diagrams of a forward-biased and reverse-biased $p - n$ junction diode. Draw the characteristics and explain it. 3+2+5
3. (a) What is the quiescent point of a transistor?
- (b) Draw the circuit diagram of a C-E transistor amplifier and explain its operation graphically.
- (c) What is a load line? Explain its significance. 2+6+2
4. (a) Why a field-effect transistor is called a unipolar device?
- (b) With a neat sketch, describe the construction of an n -channel JFET. Explain its operation.
- (c) Explain the drain characteristics of an n -channel JFET. What is the transfer characteristic? 1+4+5
5. (a) What should be the input resistance, output resistance voltage gain and bandwidth of an OPAMP?
- (b) How an OPAMP can be used as a current to voltage converter? 6+4

Please Turn Over

6. (a) Explain with a neat circuit the operation of a monostable multivibrator.
- (b) How can you convert the monostable multivibrator to an astable multivibrator? 5+5
7. (a) Explain the voltage divider transistor biasing circuit and derive the expression for output voltage (V_{CE}) and input current (I_B).
- (b) Draw the circuit diagram of a CMOS NOT gate and briefly explain its operation. 6+4
8. (a) Explain the working of R-2R ladder network as Digital to Analog Converter (DAC) with appropriate circuit diagram.
- (b) Show the efficiency of a full wave rectifier is more than 80%. 6+4
-