

2023

## COMPUTER SCIENCE — HONOURS — PRACTICAL

Paper : CC-5P

(Computer Organization Lab)

Full Marks : 30

*The figures in the margin indicate full marks.*

## Marks Distribution

Experiment total	:	20
Theory + Problem design	:	05
Implementation	:	10
Output	:	03
Discussion/Conclusion	:	02
Viva voce	:	06
Lab notebook	:	04

## SET - 2

Answer *any one* question.

1. Design a logical unit capable of performing the following operation :

Selection		Function
$S_1$	$S_0$	Y
0	0	ANDing
0	1	ORing
1	0	XORing
1	1	Complement

Comparison is to be made between 2 sets of 2-bit numbers ( $A_1 A_0$  and  $B_1 B_0$ ). Show at least 1 set of output for each function.

( 2 )

Z(3rd Sm.)-Computer.Sc.-III/Pr./CC-5P/Inst./CBCSI/Set-2

2. Design a circuit capable of performing 4-bit addition and 2's complement subtraction (inputs need not be in BCD form and hence correction is not mandatory). Take at least 3 sets of data. 20
  
  3. Design a full adder using IC 74138, and verify the outputs using LED's, also record the output logic voltage levels. 20
  
  4. Construct a 4-bit synchronous counter. using JK or D flip-flops. Use de-bouncer circuit as manual clock. 20
  
  5. Design 2-bit bidirectional shift register. (control  $\bar{R}/L$ ). De-bouncer circuit to be used as manual clock. Take at least 3 sets of data. 20
  
  6. Convert Gray to Binary code using RAM IC 7489/74189. Take at least 4 sets of data. 20
  
  7. Construct a 2-bit universal shift register using D flip-flop (7474) and 4 to 1 multiplexer (74153) with other necessary logic gates. Use a de-bouncer circuit as manual clock. 20
  
  8. Design a  $16 \times 8$  memory module using necessary logic gates and RAM IC 7489/74189. 20
-