

2025

COMPUTER SCIENCE — HONOURS

Paper : DSCC-1

(Computer Fundamentals and Digital Logic)

Full Marks : 75

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

1. Answer **any five** questions : 2×5
- (a) What is the main difference between a sequential and a combinational circuit?
 - (b) State De-Morgan's theorems.
 - (c) What is the difference between a pulse and a clock?
 - (d) Compare among Super, Mainframe and Personal computers.
 - (e) What is an implementation table?
 - (f) State difference between SOP and POS.
 - (g) Convert $(10110100)_2$ to decimal equivalent.
 - (h) What is ASCII code?

Answer **any three** questions.

2. Design a 3-bit full subtractor using basic logic gates. 5
3. Show that NAND is a universal logic gate. 5
4. Draw the circuit diagram of a 3-bit full-adder using two 4×1 MUX. 5
5. (a) What is S-R flip-flop? Draw the circuit diagram of S-R flip-flop and explain its function with truth table.
- (b) Draw the circuit diagram of a de-bouncer. 3+2
6. Implement a multiplier ($A_1 A_0$ multiplied by $B_1 B_0$) circuit and explain. 5

Please Turn Over

(5495)

Answer *any five* questions.

7. (a) Design a parity checker and generator circuit for 3-bit data.
(b) Explain how one can overcome the race around condition for a JK flip-flop. Give diagram. 5+5
8. (a) Design a synchronous MOD-5 DOWN counter.
(b) Show the timing diagram. 7+3
9. Implement the function :
(a) $F(A, B, C, D) = \sum (1, 4, 6, 10, 12, 14)$ using 16 : 1 MUX.
(b) Implement the above function by 8 : 1 MUXs. 4+6
10. (a) Draw the circuit diagram of an adder/subtractor unit. Explain its operation.
(b) Implement XOR using NAND or NOR gates. 7+3
11. (a) What are the different types of registers?
(b) Explain the operation of shift left and shift right registers. 4+6
12. (a) Minimize the function using K-map $Y = \sum_m (1, 2, 6, 7, 8, 13, 14, 15) + \sum_d (3, 5, 12)$ and draw the circuit using logic gates.
(b) Simplify the following expression using K-map in POS form $Y = \pi(3, 5, 7, 8, 10, 11, 12, 13)$. 6+4
13. (a) Draw the circuit diagram of a Master-slave J-K flip-flop and explain its operation.
(b) What is the utility of Toggle Flip-Flop? 8+2
14. Write notes on (*any two*) : 5×2
(a) ROM
(b) Clock and latch
(c) CACHE
(d) Parallel adder.
-