

2025

ELECTRONICS — MDC

Paper : CC-1

(Fundamental of Circuit Theory and Electronic Devices)

Full Marks : 75

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer **any ten** questions from **Group - I**, **any three** questions from **Group - II** and
any four questions from **Group - III**.

Group - I

1. Answer **any ten** questions : 2×10
- (a) Define active and passive circuit elements with one example of each.
 - (b) What is reverse saturation current?
 - (c) What are the typical values of the internal resistances of an ideal voltmeter and an ideal ammeter?
 - (d) State Superposition Theorem.
 - (e) What is meant by quality factor (Q-factor) of a resonant circuit?
 - (f) Distinguish between intrinsic and extrinsic semiconductors.
 - (g) Define mobility of charge carriers.
 - (h) Why is silicon preferred in integrated circuit (IC) fabrication?
 - (i) What is Early effect?
 - (j) Define ripple factor of a rectifier.
 - (k) What is pinch-off voltage in a JFET?
 - (l) Define transconductance of a MOSFET.

Group - II


Answer **any three** questions.

2. (a) Derive the expression for the growth of current in a DC RL circuit at a time t after the switch is turned on.
- (b) Define time constant of the RL circuit. 4+1

Please Turn Over

(5661)

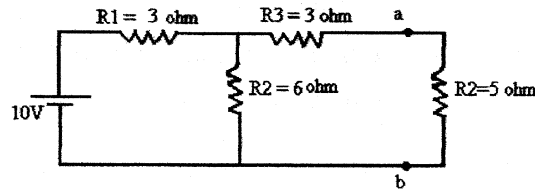3. Explain the formation of a p-n junction with a suitable diagram. Discuss the concept of depletion region and barrier potential. 2+3
4. Using Kirchhoff's laws, determine the mesh currents in the following two-loop resistive circuit : 5




5. Explain the working principle of a Zener diode. How does it act as a voltage regulator? 3+2
6. (a) Why is BJT called a bipolar device?
 (b) Draw the doping profiles of emitter, base and collector regions of a BJT. 2+3


Group - III

Answer *any four* questions.

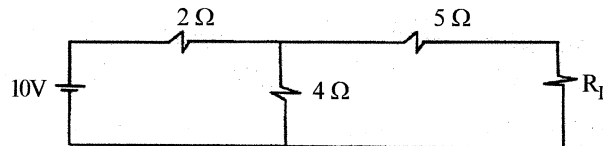7. (a) Determine the Norton's equivalent of the following circuit and find the current through the load resistance (R_L), when R_L is 15Ω .



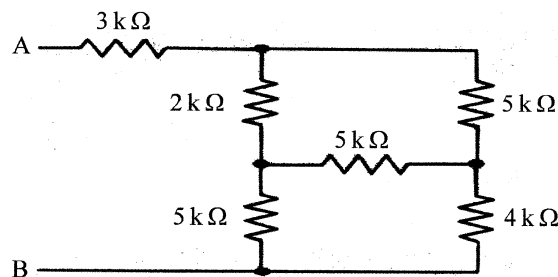- (b) Determine the equivalent resistance of the following circuit between A and B :



5+5

8. (a) Derive the expression for resonance frequency of a series RLC circuit.
 (b) Define bandwidth and show that bandwidth = R/L for a series resonant circuit.
 (c) What is selectivity of a resonant circuit? 4+4+2

9. (a) Draw and explain the working principle of a full wave rectifier.
(b) Compare a full wave rectifier with a bridge rectifier.
(c) What are load regulation and line regulation? 4+2+(2+2)
10. (a) Derive the relation between α and β of a transistor.
(b) A transistor has $\alpha = 0.98$. Calculate β .
(c) Explain the concept of thermal runaway in a transistor. 4+3+3
11. (a) Compare current gain, voltage gain, input and output impedances of BJT amplifiers in CB, CE and CC modes.
(b) Why JFET is called a unipolar device?
(c) Draw the circuit symbols of a p-channel and an n-channel JFET. What is the meaning of the arrow heads in the symbols? (2+2+2)+2+(1+1)
12. (a) Explain the construction and working of an n-channel enhancement MOSFET.
(b) Draw and explain its drain and transfer characteristics. 5+5
-