

2026

PHYSICS — HONOURS

Paper : DSCC-13

(Electronics - II)

Full Marks : 75


*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*1. Answer **any five** questions :

3×5

- Subtract $(1011)_2$ from $(11100)_2$ using 2's complement method of subtraction.
- Draw circuit diagram of OR gate using n-p-n transistors and resistances.
- Implement the boolean expression $X = AB + \bar{A}C$ using NAND gates only.
- Cascade two half adders to construct a full adder.
- Design a 8:1 multiplexer using two 4:1 multiplexers.
- Draw the circuit diagram of a clocked SR-Flip-Flop.
- What is the output after two clock pulses for a bit sequence 1101 serially entered into a 4-bit parallel-out shift register which is initially clear?
- Design a twisted ring counter (4-bit).

Answer **any five** questions.2. (a) Evaluate the sum of $(8)_{16} + (F)_{16} = (?)_{16}$.(b) Design a NOT-gate using a transistor ($\beta_{\text{sat}} = 50$) considering $V_{\text{CE sat}} = 0.2\text{V}$, $I_C = 5\text{ mA}$ and source voltage = 5 volt., $V_{\text{BE (ON)}} = 0.8\text{ V}$.

 (c) Obtain the Boolean expression for the output Y in the following logic circuit :



Simplify the expression and show that the circuit is equivalent to an AND gate with inputs A and B. Construct it using NAND gates only.

2+4+(3+2+1)

Please Turn Over

(6178)

3. (a) Simplify the following Boolean expression in SOP form using Karnaugh Map :

$$F(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 8, 9, 11, 13, 15).$$

- (b) Implement the above simplified expression using basic gates.
- (c) Implement XOR gate using NOR gates only and give its truth table.
- (d) Prove the Boolean expression : $\bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC = B$. 3+2+(3+2)+2
4. (a) Draw the full subtractor circuit using basic gate only. Also, write its truth table.
- (b) Draw the block diagram of a 4-bit binary adder subtractor and explain its operation.
- (c) Differentiate between combinational and sequential circuits with two examples each. (2+2)+4+(2+2)
5. (a) Implement the following Boolean expression using 8:1 multiplexer :
- $$F(A, B, C) = \sum m(2, 4, 6, 7)$$
- How can you use a 8:1 multiplexer to implement a logical expression with four inputs?
- (b) What is a demultiplexer? Draw the block diagram of a 4 to 16 line demultiplexer.
- (c) For a design of (16:1) multiplexer, how many select lines will be required? (3+2)+(3+2)+2
6. (a) What is the basic difference between SR Flip-Flop and JK Flip-Flop?
- (b) Draw the circuit diagram of JK Flip-Flop and explain its operation using sequence table.
- (c) Implement a D-Flip-Flop using JK Flip-Flop.
- (d) Convert an SR Flip-Flop into a JK Flip-Flop. [circuit diagram only] 2+(2+3)+3+2
7. (a) What is the basic difference in operation between MS-JK and JK Flip-Flop? Explain with block diagram.
- (b) Why is JK Flip-Flop called an one-bit register? Explain the utility of PRESET and CLEAR operation in Flip-Flop in this regard.
- (c) What is the difference between positive and negative edge triggering? Which type of triggering can be implemented using these triggering? (2+2)+(2+2)+(2+2)
8. (a) What do you mean by a counter?
- (b) Design a 4-bit ripple counter using JK Flip-Flop. Convert it into MOD-10 counter.
- (c) Draw the block diagram of a 4-bit SISO type shift register and explain its operation using sequence table. 2+(3+2)+(2+3)
9. (a) Draw the block diagram of D/A conversion circuit.
- (b) A 5-bit D/A converter produces $V_{out} = 0.2V$ for a digital input of 00001. Find the value of V_{out} for an input 1111.
- (c) "A synchronous counter is faster than an asynchronous counter" — Justify the statement.
- (d) Design a 3-bit synchronous counter and explain its operation. 3+3+2+(2+2)